



MAKER JOURNAL

Name: _____

Date: _____

Unit: Electrical Engineering Board Game Challenge

Lesson 6: Slowing the Flow with Resistors

Write a paragraph in the box below that addresses the prompt. After 2-3 minutes, be ready to share your ideas!

Quick Write Prompt: “Resistors are important in a circuit because ...”



MAKER JOURNAL

Name: _____

Date: _____

Use the table below to draw circuits and conduct calculations.

Total (Equivalent) Resistance Calculations	
Draw a circuit with two resistors in series	Draw a circuit with two resistors in parallel
Resistor Values: 100R, 22K, 56R, 470K, 1K, 220R	
<p><u>Series Circuit:</u> Choose two values from above and calculate $R_{(eq)}$. Do it again for two different values. Show your work!</p> $R_{(eq)} = R_1 + R_2$ <p>$R_{(eq)} =$ _____</p> <p>$R_{(eq)} =$ _____</p> <p><u>Ohm's Law: $V = IR$</u> Solve this formula for current (I) and calculate the current for each $R_{(eq)}$ value above. Assume a voltage of 3V.</p>	<p><u>Parallel Circuit:</u> Use the values for the series circuit to calculate $R_{(eq)}$. Show your work!</p> $1/R_{(eq)} = 1/R_1 + 1/R_2$ <p>$R_{(eq)} =$ _____</p> <p>$R_{(eq)} =$ _____</p> <p><u>Ohm's Law: $V = IR$</u> Solve this formula for current (I) and calculate the current for each $R_{(eq)}$ value above. Assume a voltage of 3V.</p>

MAKER JOURNAL

Name: _____

Date: _____

Investigation: Use the table below to record calculations and observations.

	R1 (Ω)	R2 (Ω)	R(eq) (Ω)	Voltage (V)	Current (amps)	Observations
Control	1K	None	$R(eq) = 1K = 1000 \text{ ohms}$	3V		Answers vary
Series	1K			3V		
	1K			3V		
	1K			3V		
	1K			3V		
Parallel	1K			3V		
	1K			3V		
	1K			3V		
	1K			3V		